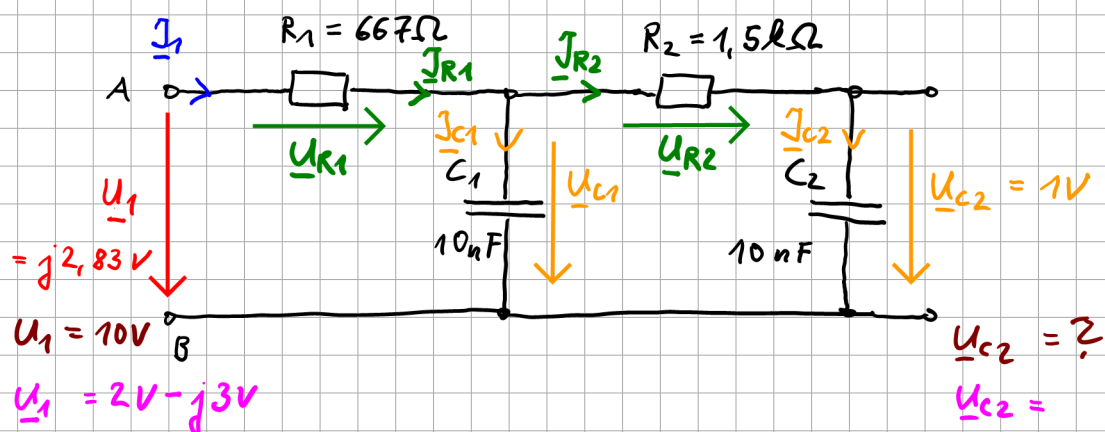


Kap. 6: Konstruktion von maßstäblichen Zeigerdiagrammen




$$f = 15,915 \text{ kHz}$$

Vorgabe: $U_{C2} \hat{=} 5 \text{ cm}$

$$J_{c2} \leq 5 \text{ cm}$$

$$u_{c2} = ?$$

$$V_{C2} =$$

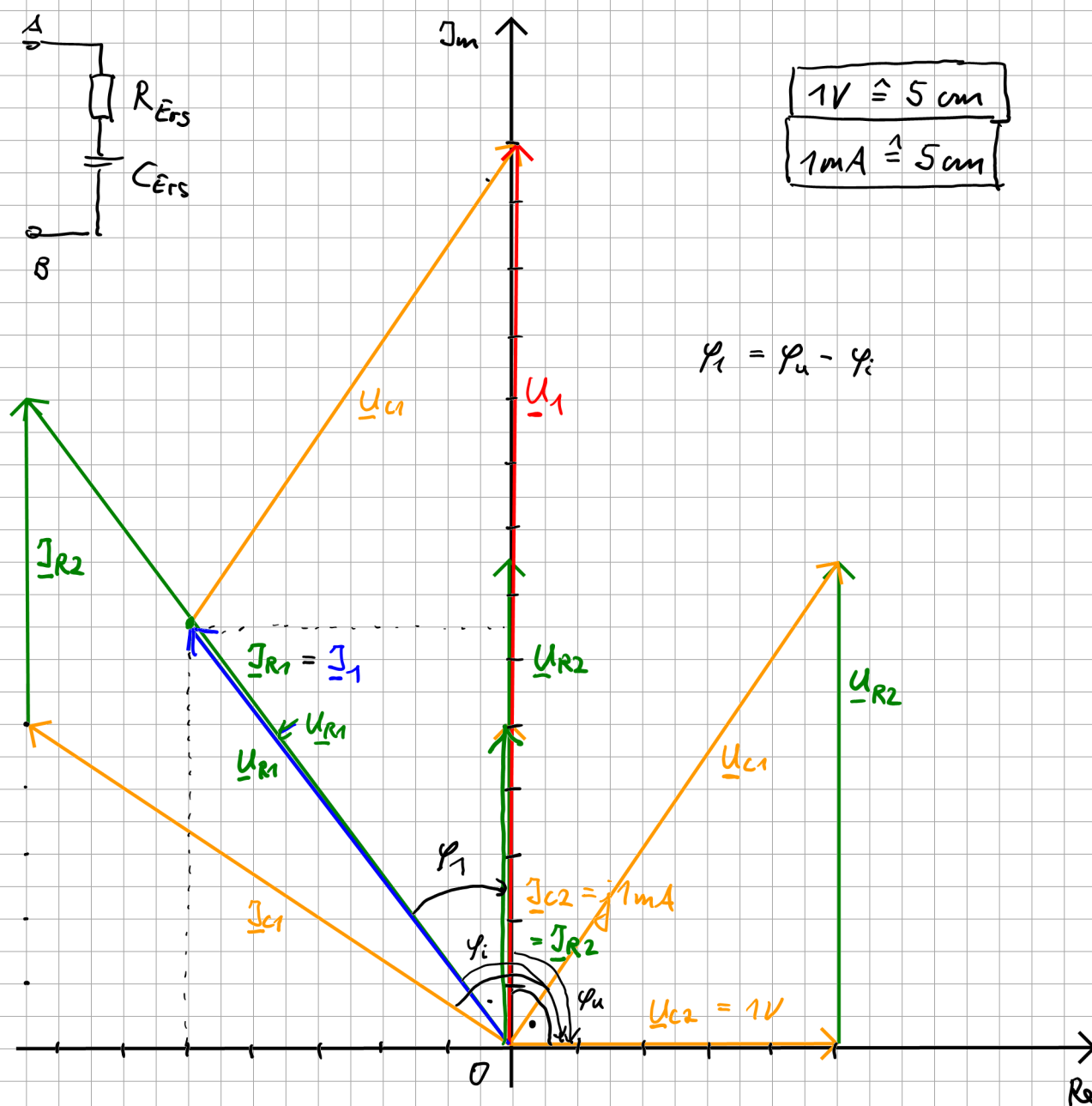

Kreisfrequenz:

$$\omega = 2\pi \cdot f = 2\pi \cdot 15,915 \text{ kHz} = 100000 \cdot \frac{1}{5} = 10^5 \cdot \frac{1}{5}$$

Bestimmung der Impedanzen:

$$\underline{Z}_{C1} = \frac{1}{j\omega C_1} = \frac{1}{j \cdot 10^5 \cdot \frac{1}{5} \cdot 10 \text{ nF}} = \frac{1}{j \cdot 1000 \cdot \frac{1}{5} \frac{\text{As}}{\text{V}}} =$$

$$= -j \cdot 1 \text{ k}\Omega$$

$$\underline{Z}_{C2} = \underline{Z}_{C1} = -j \cdot 1 \text{ k}\Omega$$

$$\underline{I}_{C2} = \frac{\underline{U}_{C2}}{\underline{Z}_{C2}} = \frac{1 \text{ V}}{-j \cdot 1 \text{ k}\Omega} = +j \cdot 1 \text{ mA} \quad (\hat{=} 5 \text{ cm})$$

Vorgabe

$$\underline{I}_{R2} = \underline{I}_{C2}$$

$$\underline{U}_{R2} = R_2 \cdot \underline{I}_{R2}$$

$$= 1,5 \text{ k}\Omega \cdot j \cdot 1 \text{ mA}$$

$$= j \cdot 1,5 \text{ V} \quad (\hat{=} 7,5 \text{ cm})$$

$$\underline{U}_{C1} = \underline{U}_{R2} + \underline{U}_{C2}$$

$$= j \cdot 1,5 \text{ V} + 1 \text{ V}$$

$$= 1 \text{ V} + j \cdot 1,5 \text{ V}$$

$$\underline{I}_{C1} = \frac{\underline{U}_{C1}}{\underline{Z}_{C1}}$$

$$= \frac{1 \text{ V} + j \cdot 1,5 \text{ V}}{-j \cdot 1 \text{ k}\Omega} = \frac{1 \text{ V}}{-j \cdot 1 \text{ k}\Omega} + \frac{j \cdot 1,5 \text{ V}}{-j \cdot 1 \text{ k}\Omega}$$

$$= +j \cdot 1 \text{ mA} - 1,5 \text{ mA}$$

$$\underline{I}_1 = \underline{I}_{R1} = \underline{I}_{C1} + \underline{I}_{R2}$$

$$= j \cdot 1 \text{ mA} - 1,5 \text{ mA} + j \cdot 1 \text{ mA}$$

$$= -1,5 \text{ mA} + j 2 \text{ mA}$$

$\uparrow \text{Re} < 0$

$$= \sqrt{(-1,5 \text{ mA})^2 + (2 \text{ mA})^2} \cdot e^{j \arctan\left(\frac{2 \text{ mA}}{-1,5 \text{ mA}}\right) \pm j 180^\circ}$$

$$= 2,5 \text{ mA} \cdot e^{-j(53^\circ \pm j 180^\circ)}$$

$$= 2,5 \text{ mA} \cdot e^{+j 126,9^\circ}$$

$$\underline{U}_{R1} = R_1 \cdot \underline{I}_{R1}$$

$$= 667 \Omega \cdot (-1,5 \text{ mA} + j 2 \text{ mA})$$

$$= -1 \text{ V} + j 1,334 \text{ V}$$

$$= -1 \text{ V} + j \frac{4}{3} \text{ V}$$

$$\underline{U}_1 = \underline{U}_{R1} + \underline{U}_{C1}$$

$$= -1 \text{ V} + j \frac{4}{3} \text{ V} + 1 \text{ V} + j 1,5 \text{ V}$$

$$= j 2,833 \text{ V}$$

$$1 \text{ V} \hat{=} 5 \text{ cm}$$

$$\Rightarrow U_1 \hat{=} 14,2 \text{ cm}$$

Phasenverschiebung am Eingang

$$\varphi_1 = \varphi_u - \varphi_i$$

$$\underline{U}_1 = j 2,833 \text{ V} \Rightarrow \varphi_{u1} = 90^\circ$$

$$\underline{I}_1 = 2,5 \text{ mA} \cdot e^{j 126^\circ} \Rightarrow \varphi_{i1} = 126^\circ$$

$$\varphi_1 = 90^\circ - 126^\circ$$

$$= -36^\circ$$

Linearität

$$\underline{U}_{C2} = 1 \text{ V} \Rightarrow \underline{U}_1 = j 2,83 \text{ V}$$

$\times$

$\Leftarrow$

$$\underline{U}_1 = 10 \text{ V}$$

$$\frac{\underline{U}_{C2}}{X} = \frac{j 2,83 V}{10 V}$$

$$\Rightarrow X = \frac{10 V \cdot \underline{U}_{C2}}{j 2,83 V} = \frac{10 V \cdot 1 V}{j 2,83 V} = 3,53 V \frac{1}{j} = -j 3,53 V$$

$$\underline{U}_1 = j 2,83$$

$$\underline{U}_{C2} = 1 V$$

$$\underline{U}_1 = 2 V - j 3 V$$

$$\underline{U}_{C2} = X$$

$$\frac{j 2,83 V}{2 V - j 3 V} = \frac{1 V}{X}$$

$$\Rightarrow X = \frac{(2 V - j 3 V) \cdot 1 V}{j 2,83 V}$$

$$= \frac{1}{j} 0,707 V - 1,06 V$$

$$= -1,06 V - j 0,707 V$$

↑ $\text{Re} < 0$

$$= \sqrt{(1,06 V)^2 + (0,707 V)^2} \cdot e^{j(\arctan\left(\frac{-0,707}{-1,06}\right) \pm 180^\circ)}$$

$$= 1,27 V \cdot e^{-j 146^\circ}$$