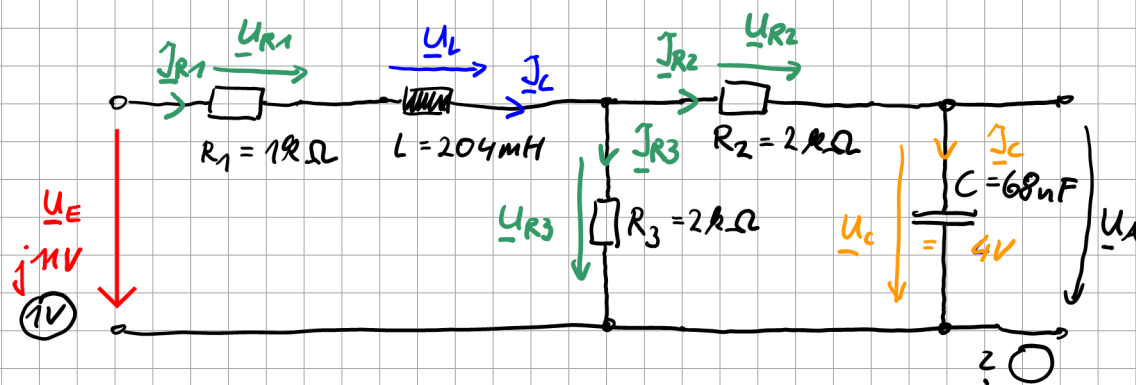


ZE11




$$\omega = 7353 \frac{1}{s}$$

$$|\underline{U}_A| \hat{=} 4cm$$

$$|\underline{I}_C| \hat{=} 4cm$$

Freie Wahl Maßstab

$1V \hat{=} 1cm$
$1mA \hat{=} 2cm$

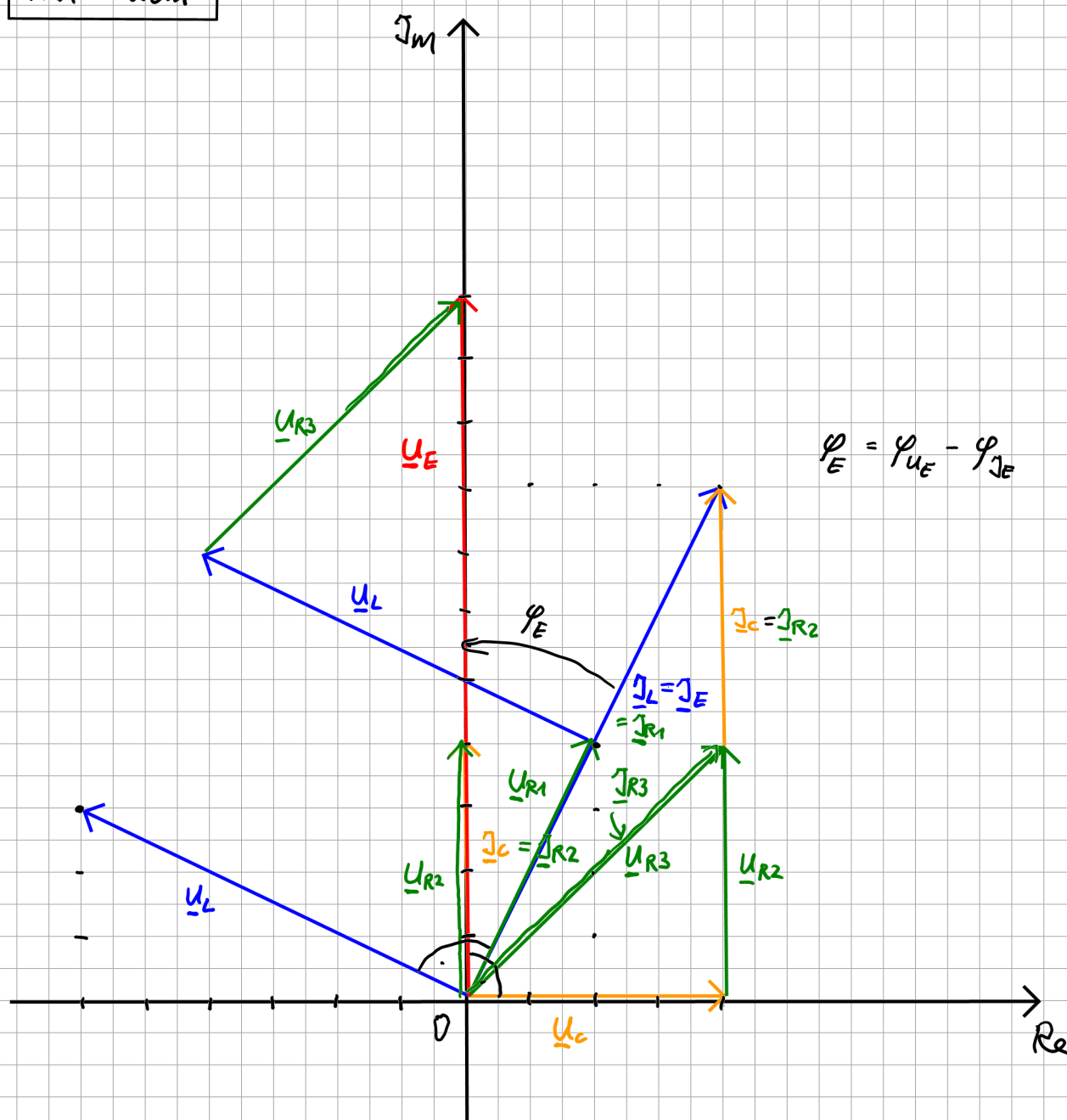

$$\underline{U}_A = \underline{U}_c = 4V + j0V \quad (\text{rechts})$$

$$\underline{I}_c = \frac{\underline{U}_c}{\underline{Z}_c}$$

$$\underline{Z}_c = \frac{1}{j\omega c} = \frac{1}{j 7353 \frac{1}{s} \cdot 68nF} = \frac{1}{j} 2000 \frac{1}{\frac{As}{Vs}} = -j 2000 \Omega = -j 2k\Omega$$

$$\underline{I}_c = \frac{4V}{-j 2k\Omega} = +j 2mA \quad (\hat{=} 4cm)$$

$\Rightarrow$ Maßstab $1mA \hat{=} 2cm$

$$\underline{I}_{R2} = \underline{I}_c = j 2mA$$

$$\begin{aligned} \underline{U}_{R2} &= R_2 \cdot \underline{I}_{R2} \\ &= 2k\Omega \cdot j 2mA = j 4V \end{aligned}$$

$$\begin{aligned} \underline{U}_{R3} &= \underline{U}_{R2} + \underline{U}_c \\ &= j 4V + 4V = 4V + j 4V \end{aligned}$$

$$\underline{I}_{R3} = \frac{\underline{U}_{R3}}{R_3} = \frac{4V + j 4V}{2k\Omega} = 2mA + j 2mA$$

$\begin{matrix} 4cm & 4cm \\ \text{rechts} & \text{oben} \end{matrix}$

$$\begin{aligned} \underline{I}_{R1} = \underline{I}_L &= \underline{I}_{R2} + \underline{I}_{R3} \\ &= j 2mA + 2mA + j 2mA \\ &= 2mA + j 4mA \end{aligned}$$

$$\underline{U}_L = \underbrace{j\omega L}_{\underline{Z}_L} \cdot \underline{I}_L$$

$$\underline{Z}_L = j\omega L = j 7353 \frac{1}{s} \cdot 204mH = j 1500\Omega$$

$$\begin{aligned} \underline{U}_L &= j 1500\Omega \cdot (2mA + j 4mA) \\ &= j 3V + j^2 6V \\ &= -6V + j 3V \end{aligned}$$

$$\begin{aligned}
 \underline{U}_{R1} &= R_1 \cdot \underline{I}_{R1} \\
 &= 1k\Omega \cdot (2mA + j4mA) \\
 &= 2V + j4V
 \end{aligned}$$

$$\begin{aligned}
 \underline{U}_E &= \underline{U}_{R1} + \underline{U}_L + \underline{U}_{R3} \\
 &= 2V + j4V - 6V + j3V + 4V + j4V \\
 &= j11V
 \end{aligned}$$

b) Ähnlichkeit

$$\underline{U}_A = 4V \quad \Rightarrow \quad \underline{U}_E = j11V$$

$$\underline{U}_A = x \quad \Leftarrow \quad \underline{U}_E = 1V$$

$$\frac{4V}{x} \hat{=} \frac{j11V}{1V}$$

$$\Rightarrow x = \frac{4V \cdot 1V}{j11V} = -j \frac{4}{11} V$$

c) $\varphi_E = \varphi_{U_E} - \varphi_{I_E}$

$$= \angle \left(\frac{\underline{U}_E}{\underline{I}_E} \right) \begin{matrix} \leftarrow \text{wohin} \\ \leftarrow \text{woher} \end{matrix}$$

$$\varphi_{U_E} = \angle(\underline{U}_E) = +90^\circ$$

$$\begin{aligned}
 \varphi_{I_E} &= \angle(\underline{I}_E) = \angle(2mA + j4mA) \\
 &= \arctan\left(\frac{4mA}{2mA}\right) = 63,4^\circ
 \end{aligned}$$


$$\varphi_E = 90^\circ - 63,4^\circ = 26,6^\circ$$

d) Wir suchen Ersatzschaltung bezüglich Eingang:

$$\underline{U_E} = j11 \text{ V}$$

$$\underline{I_E} = 2 \text{ mA} + j4 \text{ mA}$$

Parallelschaltung:

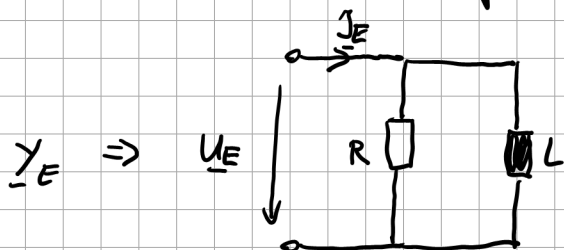

$$\underline{Y_E} = \frac{\underline{I_E}}{\underline{U_E}} = \frac{1}{R} + \frac{1}{j\omega L}$$

$$\frac{2 \text{ mA} + j4 \text{ mA}}{j11 \text{ V}} = -j \frac{2}{11} \text{ mS} + \frac{4}{11} \text{ mS} = \frac{1}{R} + \frac{1}{j\omega L}$$

$$\Rightarrow \frac{1}{R} = \frac{4}{11} \text{ mS}$$

$$R = \frac{11}{4} \text{ k}\Omega = 2,75 \text{ k}\Omega$$

$$\frac{1}{j\omega L} = -j \frac{2}{11} \text{ mS}$$

$$\cancel{j} \frac{1}{\omega L} = \cancel{-j} \frac{2}{11} \text{ mS}$$

$$\omega L = \frac{11}{2} \text{ mS}$$

$$L = \frac{1}{\omega} \cdot \frac{11}{2} \text{ k}\Omega$$

$$= \frac{1}{7353 \frac{1}{\text{s}}} \cdot \frac{11}{2} \text{ k} \frac{\text{V}}{\text{A}}$$

$$= 750 \cdot 10^{-6} \text{ mH}$$

$$= 0,75 \text{ H}$$

$$\frac{\text{Vs}}{\text{A}} = \text{H}$$

Ersatzschaltung in Reihe:

$$\underline{Z}_E = \frac{\underline{U}_E}{\underline{I}_E} = \dots = R_e + j X_m$$

$$= \frac{j 11 \text{ V}}{2 \text{ mA} + j 4 \text{ mA}}$$

$$= \frac{j 11 \text{ V}}{\sqrt{(2 \text{ mA})^2 + (4 \text{ mA})^2} \cdot e^{j \arctan\left(\frac{4 \text{ mA}}{2 \text{ mA}}\right)}}$$

$$= \frac{j 11 \text{ V}}{4,47 \text{ mA} \cdot e^{j 63,4^\circ}}$$

$$= \frac{11 \text{ V}}{4,47 \text{ mA}} e^{j 90^\circ} \cdot e^{-j 63,4^\circ}$$

$$= 2460 \, \Omega \cdot e^{j 26,6^\circ}$$

$$= 2460 \, \Omega \cdot \cos(26,6^\circ) + j 2460 \, \Omega \cdot \sin(26,6^\circ)$$

$$= 2200 \, \Omega + j 1100 \, \Omega$$

$$= R + j \omega L$$

$$\omega L = 1100 \, \Omega$$

$$L = \frac{1100 \, \Omega}{7353 \frac{1}{\text{s}}} = 0,15 \text{ H}$$