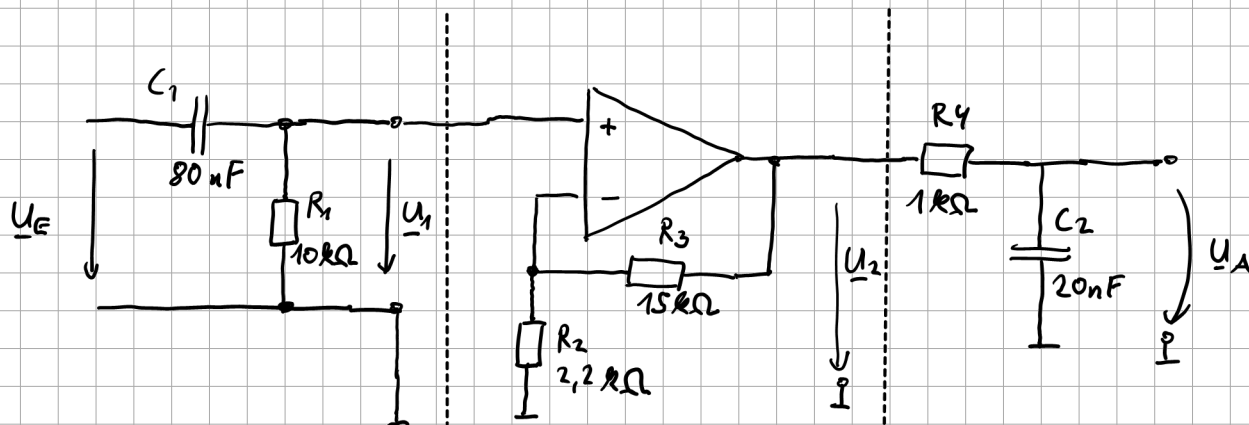


BOD 3



$$\underline{A_1} = \frac{\underline{U_1}}{\underline{U_E}} = \frac{R_1}{R_1 + \underline{Z_{C1}}}$$

$$= \frac{R_1}{\frac{1}{j\omega C_1} + R_1} \cdot \frac{j\omega C_1}{j\omega C_1}$$

$$= \frac{j\omega \underbrace{C_1 R_1}_{\tau_1}}{1 + j\omega \underbrace{R_1 C_1}_{\tau_1}}$$

$$\tau_1 = \frac{1}{\omega_1}$$

$$\omega_1 = 2\pi f_1$$

$$\underline{A_1} = \frac{j \frac{\omega}{\omega_1}}{1 + j \frac{\omega}{\omega_1}}$$

$$= \frac{j \frac{2\pi f}{2\pi f_1}}{1 + j \frac{2\pi f}{2\pi f_1}}$$

Hochpass

$$\underline{A_1} = \frac{j \frac{f}{f_1}}{1 + j \frac{f}{f_1}}$$

$$\tau_1 = R_1 \cdot C_1$$

$$= 10 \text{ k}\Omega \cdot 80 \text{ nF}$$

$$= 800 \mu\text{s}$$

$$\omega_1 = \frac{1}{\tau_1} = 1250 \frac{1}{\text{s}}$$

$$\underline{f_1} = \frac{\omega_1}{2\pi} = \underline{199 \text{ Hz}}$$

$$\underline{A_2} = \frac{\underline{U_2}}{\underline{U_1}} = 1 + \frac{R_3}{R_2}$$

$$= 1 + \frac{15 \text{ k}\Omega}{2.2 \text{ k}\Omega}$$

$$= 7.82$$

Konstante

$$K_{dB} = 20 \cdot \log 7.82$$

$$= \underline{17.9 \text{ dB}}$$

Aufgabe:

