
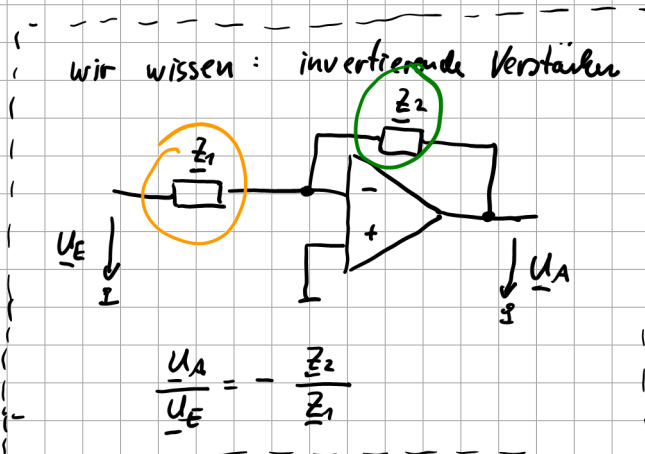
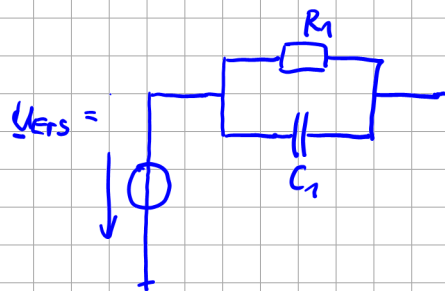
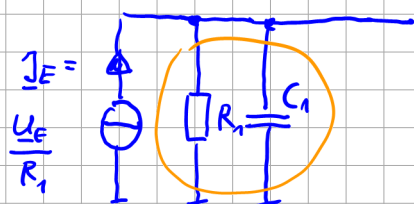
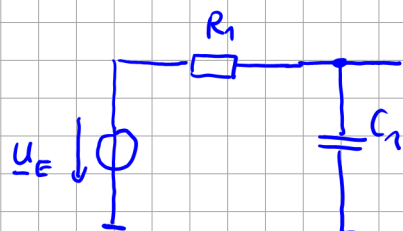



BOD 4

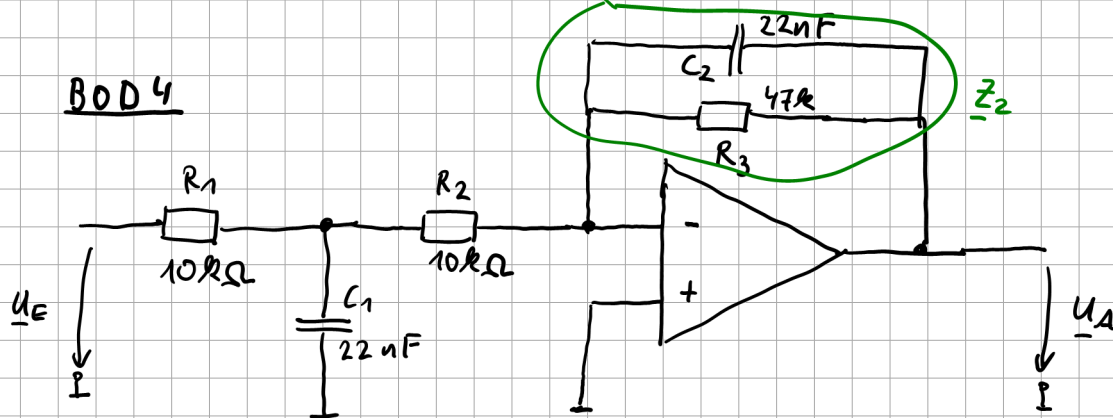

$$U_{Ers} = I_E \cdot (R_1 \parallel Z_{C1})$$

$$= I_E \cdot \frac{R_1 \cdot \frac{1}{j\omega C_1}}{R_1 + \frac{1}{j\omega C_1}} \cdot \frac{j\omega C_1}{j\omega C_1} = I_E \cdot \frac{R_1}{1 + j\omega R_1 C_1}$$
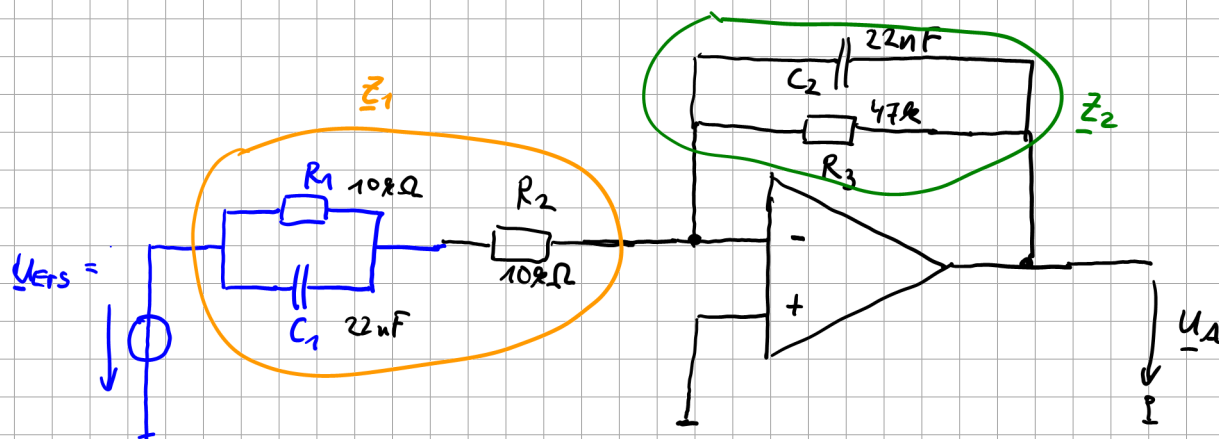
$$U_{Ers} = \frac{U_E}{R_{\Sigma}} \cdot \frac{R_{\Sigma}}{1 + j\omega R_1 C_1} = U_E \cdot \frac{1}{1 + j\omega R_1 C_1}$$



Aufgabe:

$$A_{\text{ges}} = K \cdot \frac{1}{1+j\frac{f}{f_1}} \cdot \frac{1}{1+j\frac{f}{f_2}}$$


Tiefpass TP1 Tiefpass TP2

$$K = -2,34$$

$$K_{\text{dB}} = 7,4 \text{ dB}$$

$$f_1 = 154 \text{ Hz}$$

$$f_2 = 1447 \text{ Hz}$$

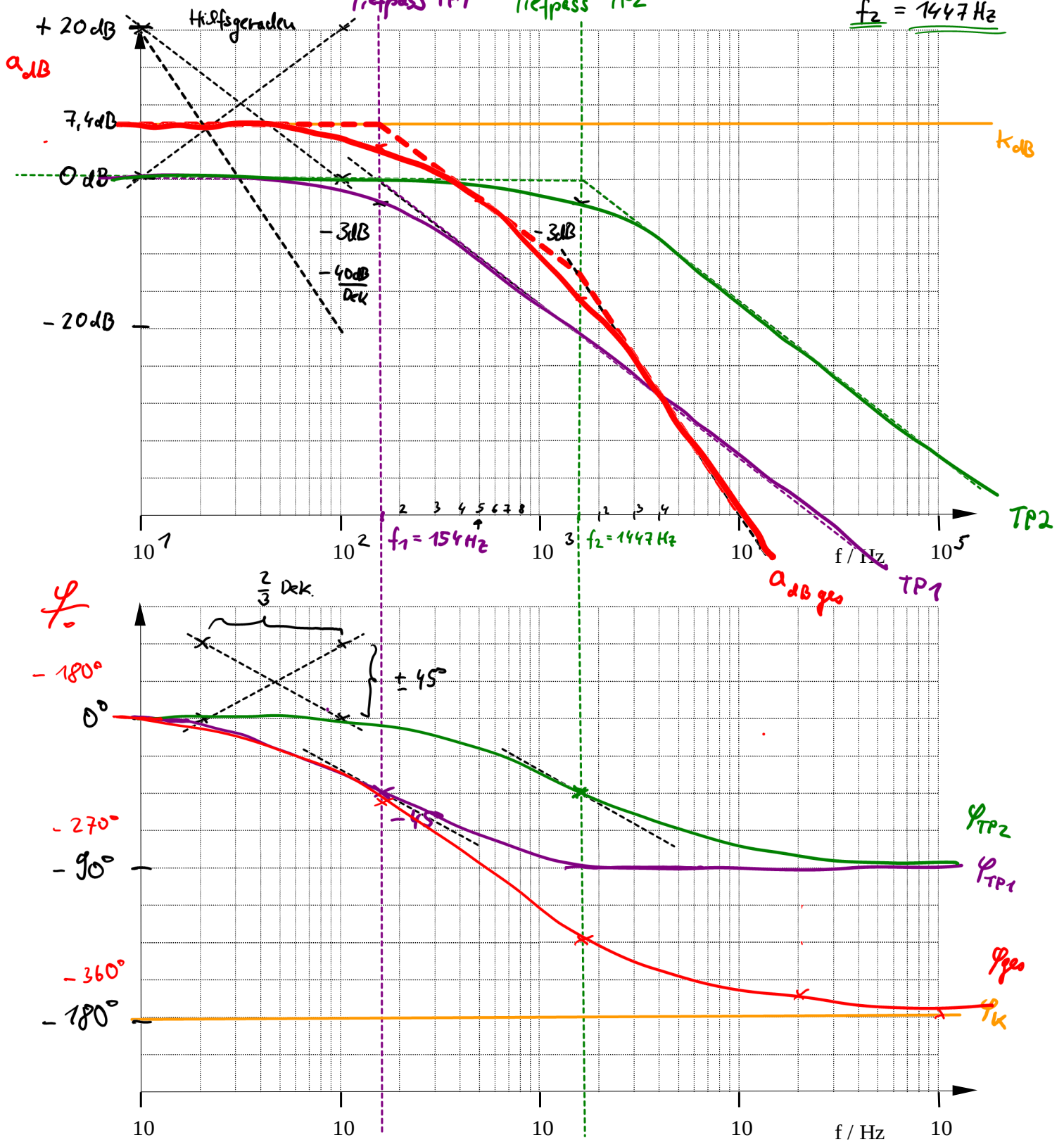

$$\underline{Z}_2 = (\underline{Z}_{C2} \parallel R_3) = \frac{\frac{1}{j\omega C_2} \cdot R_3}{\frac{1}{j\omega C_2} + R_3} = \frac{R_3}{1 + j\omega C_2 R_3}$$

$$\begin{aligned}\underline{Z}_1 &= (R_1 \parallel \underline{Z}_{C1}) + R_2 = \frac{\frac{1}{j\omega C_1} \cdot R_1}{\frac{1}{j\omega C_1} + R_1} + R_2 \\ &= \frac{R_1}{1 + j\omega C_1 R_1} + R_2 \\ &= \frac{R_1 + R_2 \cdot (1 + j\omega C_1 R_1)}{1 + j\omega C_1 R_1} \\ &= \frac{R_1 + R_2 + j\omega C_1 R_1 R_2}{1 + j\omega C_1 R_1}\end{aligned}$$

$$\begin{aligned}\frac{\underline{U}_A}{\underline{U}_{Ers}} &= - \frac{\underline{Z}_2}{\underline{Z}_1} = - \frac{\frac{R_3}{1 + j\omega C_2 R_3}}{\frac{R_1 + R_2 + j\omega C_1 R_1 R_2}{1 + j\omega C_1 R_1}} \\ &= - \frac{R_3}{(1 + j\omega C_2 R_3)} \cdot \frac{(1 + j\omega C_1 R_1)}{(R_1 + R_2 + j\omega C_1 R_1 R_2)}\end{aligned}$$

$$\frac{\underline{U}_A}{\underline{U}_E} \cdot \frac{1}{1 + j\omega R_1 C_1} = - \frac{R_3}{(1 + j\omega C_2 R_3)} \cdot \frac{(1 + j\omega C_1 R_1)}{(R_1 + R_2 + j\omega C_1 R_1 R_2)} \cdot \frac{1}{1 + j\omega R_1 C_1}$$

$$\frac{\underline{U}_A}{\underline{U}_E} = - \frac{R_3}{1 + j\omega \underbrace{C_2 R_3}_{T_1}} \cdot \frac{1}{(R_1 + R_2) + j\omega C_1 R_1 R_2}$$

b) $A_{ges}(j\omega) = \underbrace{K}_{\text{Vorgabe}} \cdot \frac{1}{(1 + j\frac{\omega}{\omega_1}) \cdot (1 + j\frac{\omega}{\omega_2})}$

$$\begin{aligned}\frac{\underline{U}_A}{\underline{U}_E} &= - R_3 \cdot \frac{1}{1 + j\omega C_2 R_3} \cdot \frac{1}{R_1 + R_2} \cdot \frac{1}{1 + j\omega C_1 \frac{R_1 R_2}{R_1 + R_2}} \\ &= - \frac{R_3}{R_1 + R_2} \cdot \frac{1}{1 + j\omega \underbrace{C_2 R_3}_{T_1}} \cdot \frac{1}{1 + j\omega \underbrace{C_1 \frac{R_1 R_2}{R_1 + R_2}}_{T_2}}\end{aligned}$$

Zahlenwerte:

$$K = - \frac{R_3}{R_1 + R_2} = - \frac{47k}{10k + 10k} = -2,35$$

$$\underline{K_{dB}} = 20 \cdot \log_{10} |-2,35| = \underline{7,4 \text{ dB}}$$

$$\tau_1 = C_2 R_3 = 22 \mu F \cdot 47 k\Omega = 1,034 \text{ ms}$$

$$\omega_1 = \frac{1}{\tau_1} = 967 \frac{1}{s}$$

$$\underline{f_1 = \frac{\omega_1}{2\pi} = 154 \text{ Hz}}$$

$$\tau_2 = C_1 \cdot \frac{R_1 R_2}{R_1 + R_2} = 22 \mu F \cdot \frac{10 k\Omega \cdot 10 k\Omega}{10 k\Omega + 10 k\Omega} = 110 \mu s$$

$$\omega_2 = \frac{1}{\tau_2} = 9091 \frac{1}{s}$$

$$\underline{f_2 = \frac{\omega_2}{2\pi} = 1447 \text{ Hz}}$$

$$\frac{U_A}{U_E} = \underbrace{- \frac{R_3}{R_1 + R_2}}_K \cdot \underbrace{\frac{1}{1 + j \frac{f}{f_1}}}_{TP1} \cdot \underbrace{\frac{1}{1 + j \frac{f}{f_2}}}_{TP2}$$

c) Grenzwerte bestimmen für $\omega \rightarrow 0$, $\omega \rightarrow \infty$

$$\lim_{\omega \rightarrow 0} A(j\omega) = \lim_{\substack{\omega \rightarrow 0 \\ f \rightarrow 0}} \left(- \frac{R_3}{R_1 + R_2} \cdot \frac{1}{1 + j \frac{f}{f_1}} \cdot \frac{1}{1 + j \frac{f}{f_2}} \right)$$

Vorgehen $\hat{=}$ "1 + j \frac{f}{f_1}"

$$= \ominus \frac{R_3}{R_1 + R_2} \quad \varphi = \pm 180^\circ$$

$$\varphi(\omega \rightarrow 0) = \pm 180^\circ$$



$$\lim_{\substack{\omega \rightarrow \infty \\ f \rightarrow \infty}} A(j\omega) = \lim_{f \rightarrow \infty} \left(\cancel{\frac{R_3}{R_1 + R_2}} \cdot \frac{1}{\cancel{j} \frac{f}{f_1}} \cdot \frac{1}{\cancel{j} \frac{f}{f_2}} \right)$$

$$= \lim_{f \rightarrow \infty} \left(\frac{R_3}{R_1 + R_2} \cdot \frac{f_1 \cdot f_2}{f^2} \right)$$



$$= 0$$

$$\varphi(\omega \rightarrow \infty) = 0^\circ$$

Aufgabe:

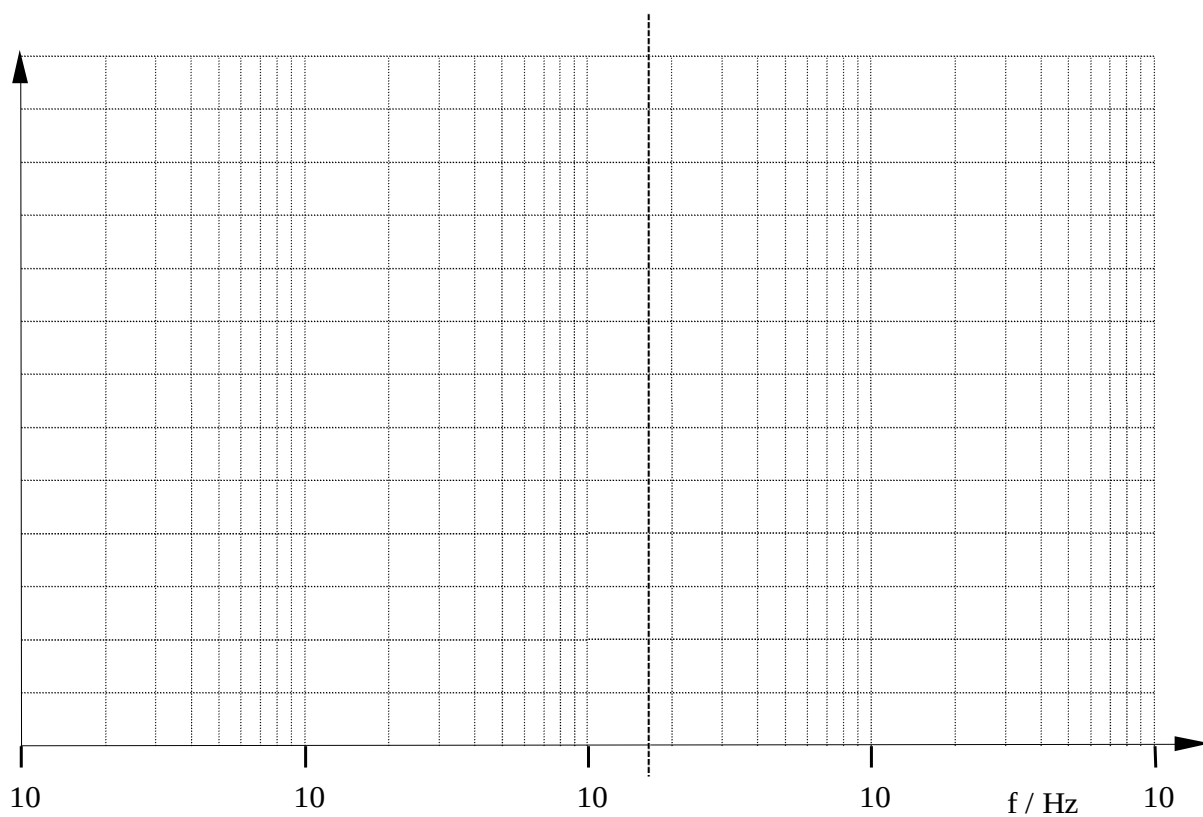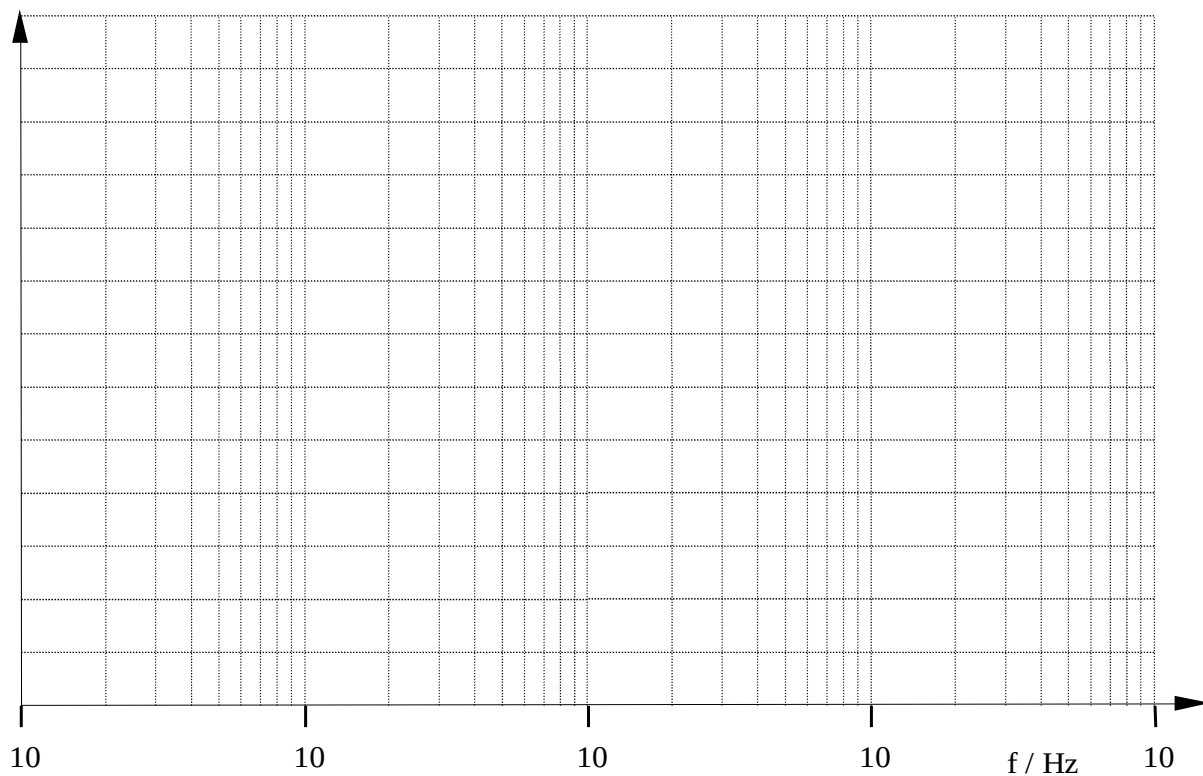

Aufgabe:

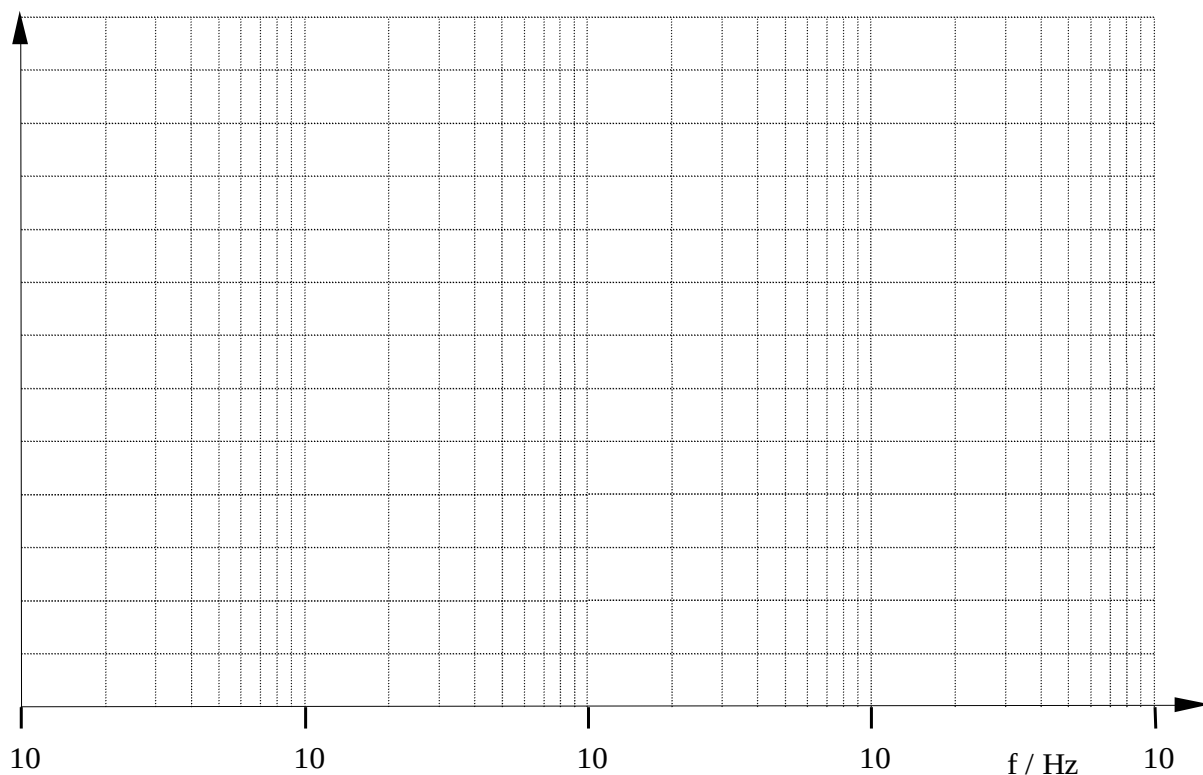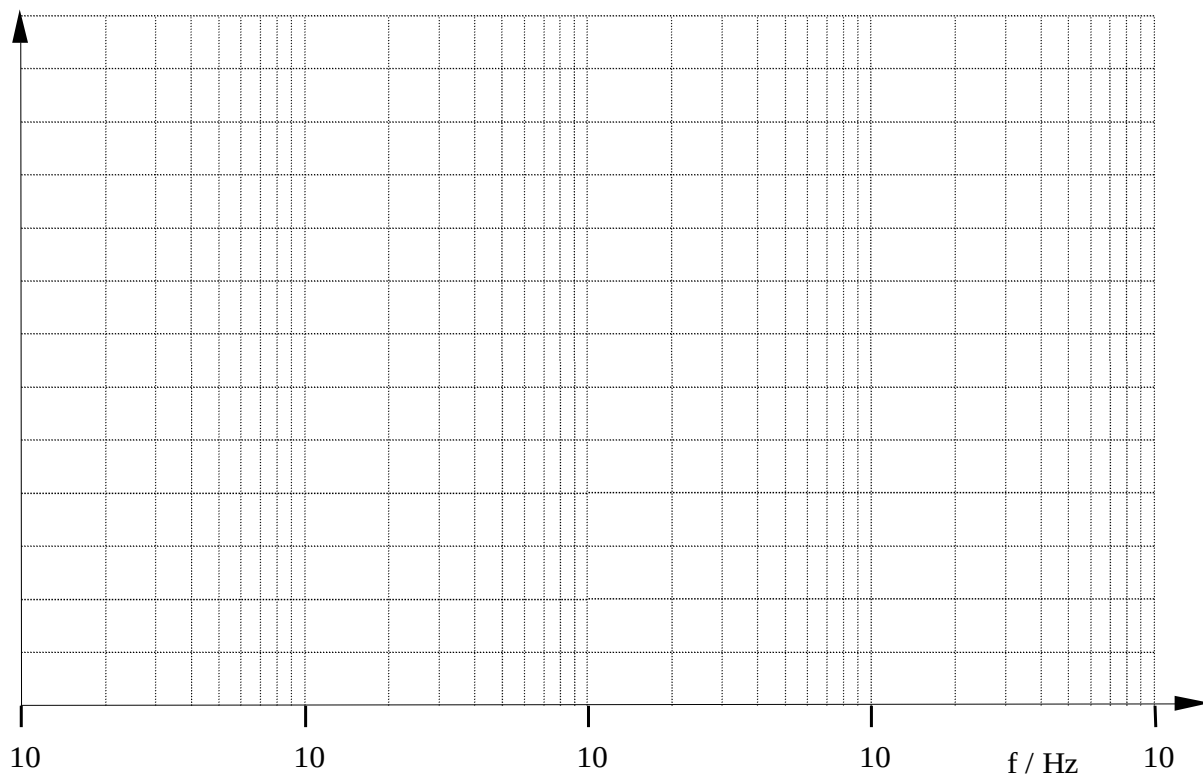

Aufgabe:

